

INDEX

SN	Title	Page No.	Date	Signature
1.	Familiarizing with the syntax, data types, and operators of VHDL.	1-2	2081/01/08	
2.	Design of Basic Logic Gates using VHDL	3-6	2081/01/08	
3.	Design of Half Adder and Full Adder using VHDL	7-9	2081/01/08	
4.	Design of Multiplexer and De multiplexer using VHDL	10-13	2081/01/08	
5.	Design 4-bit binary-to-gray and gray-to-binary code converters using VHDL	14-17	2081/01/09	
6.	Design 8-bit parity generator and checker circuits using VHDL	18-22	2081/01/09	
7.	Design Encoder and Decoder using VHDL	23-27	2081/01/09	
8.	Design 2's Complement Adder-Subtractor using VHDL	28-30	2081/01/09	
9.	Design of Registers using VHDL (SR flip-flop or JK flip-flop or D flip-flop or T flip-flop)	31-33	2081/01/10	
10.	Design 4-bit ALU using VHDL	34-36	2081/01/10	
12.	Simulation of 5 stage or 4 stage or 3 stage pipelining	37-41	2081/01/11	
13.	Simulation of Booth addition and subtraction of signed 2's complement data. (Implement using VHDL or C)	42-45	2081/01/11	
14.	Simulation of Boot multiplication and division algorithm. (Implement using VHDL or C program)	46-55	2081/01/11	